

S4

SMALL SATELLITES FOR SECONDARY STUDENTS

Introduction to Electronics



Prof. Lynn Cominsky






Ohm's Law

- Summarizes the relationship between Potential Difference (V), resistance (R) and current (I)
- Potential difference is measured in volts (V)
- Resistance is measured in ohms (Ω)
- Current is measured in amperes (A)

$$V = IR$$

Resistor Color Code

Color	Band 1	Band 2	Band 3
Black	0	0	1.00
Brown	1	1	10.00
Red	2	2	100.00
Orange	3	3	1,000.00
Yellow	4	4	10,000.00
Green	5	5	100,000.00
Blue	6	6	1,000,000.00
Violet	7	7	10,000,000.00
Grey	8	8	
White	9	9	
Gold			0.10
Silver			0.01

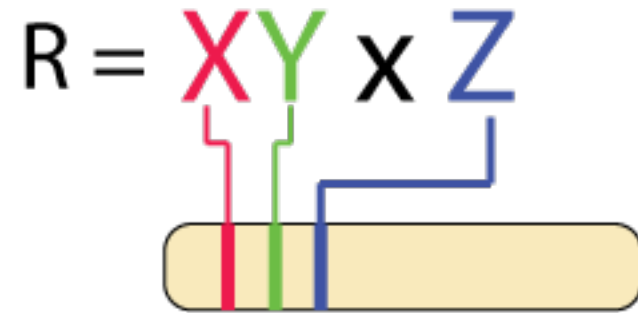


What is
this
resistance?

Brown → 1
Green → 5
Brown → x 10
= 150 Ω

Series Resistors

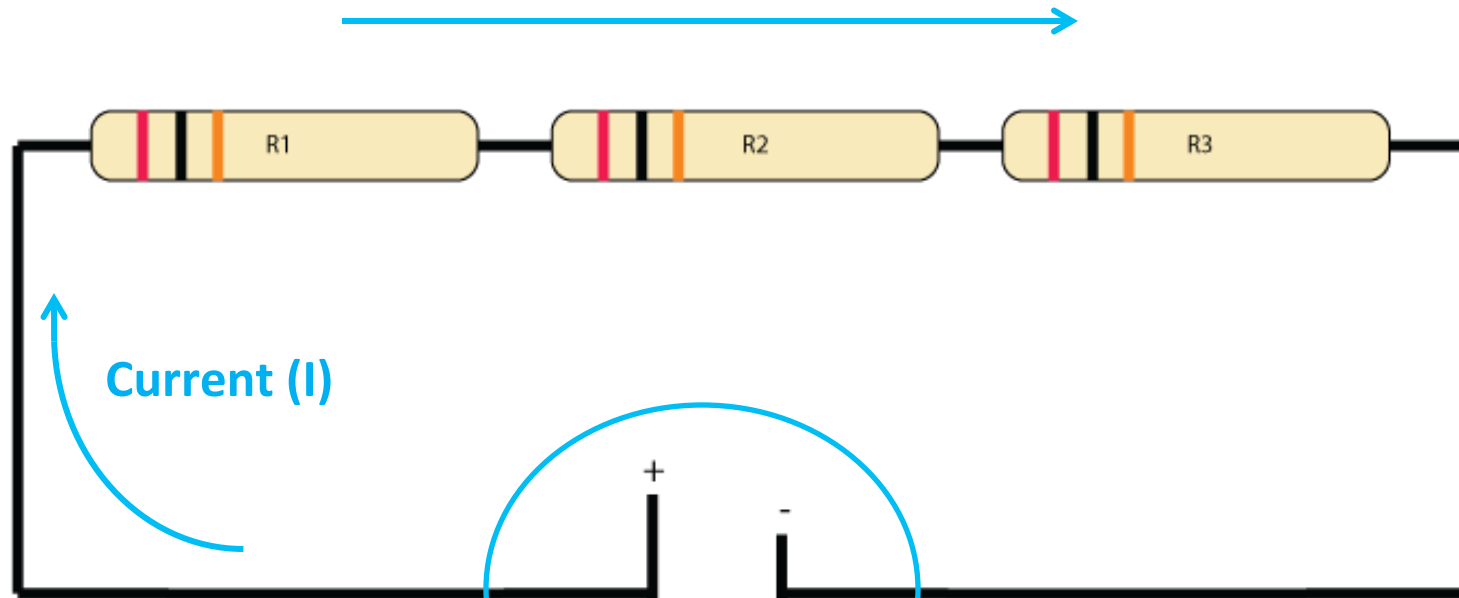
Same current flows through all 3 resistors



$$V = I R_{\text{tot}}$$
$$R_{\text{tot}} = R1 + R2 + R3$$

Symbol for a
battery or voltage
source (V)

Parallel resistors

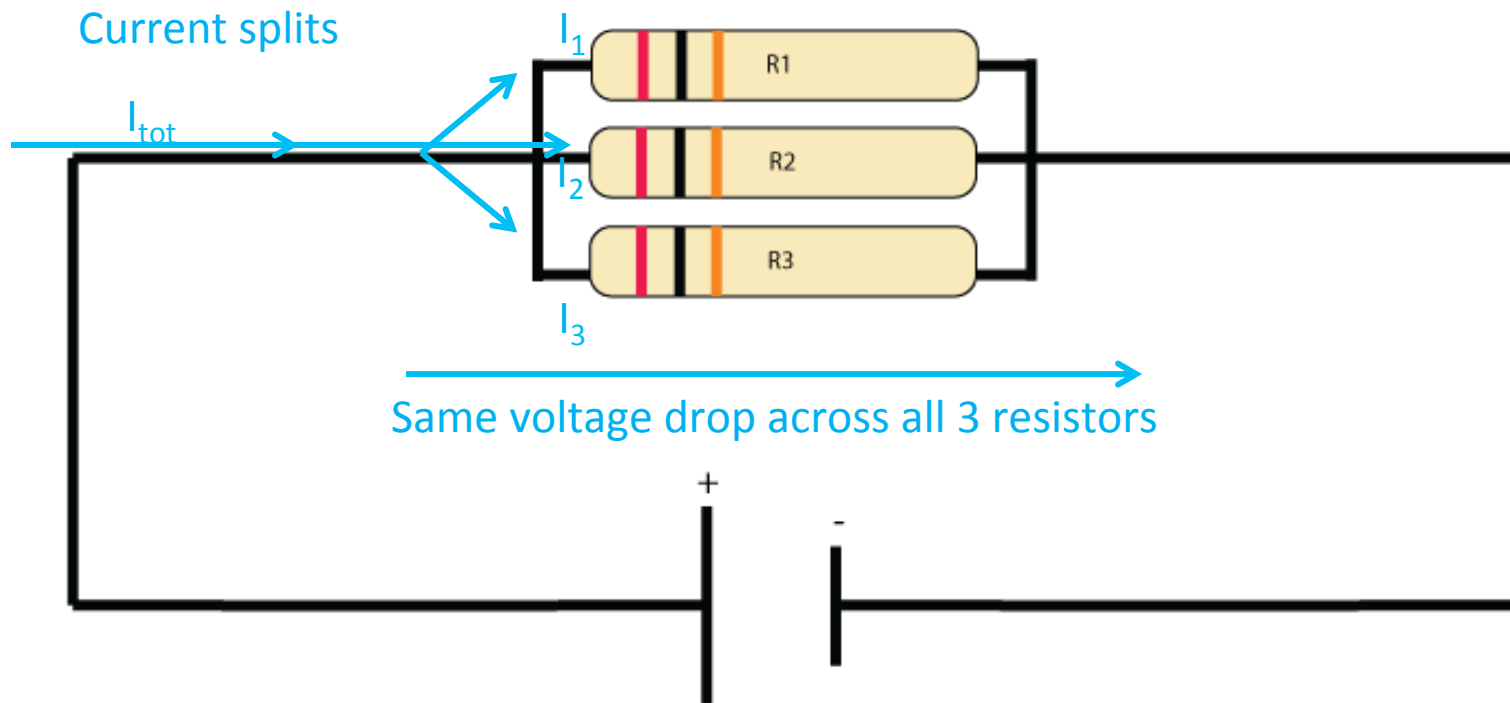

$$V = I_{tot} R_{eq}$$

$$V = I_1 R_1 = I_2 R_2 = I_3 R_3$$


$$I_{tot} = I_1 + I_2 + I_3$$

$$1/R_{eq} = 1/R_1 + 1/R_2 + 1/R_3$$

Capacitors in Parallel

definition of
capacitance:

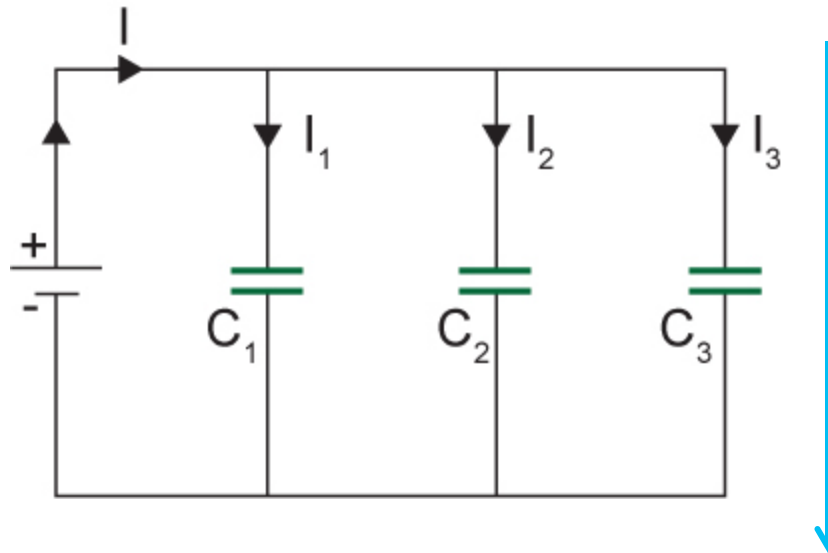$C = Q/V$ where Q is the
charge held on a plate




$$V = Q_{\text{tot}} / C_{\text{tot}}$$

$$V = Q_1 / C_1 = Q_2 / C_2 = Q_3 / C_3$$

$$C_{\text{tot}} = Q_1 / V + Q_2 / V + Q_3 / V$$

$$C_{\text{tot}} = C_1 + C_2 + C_3$$

Capacitors in series

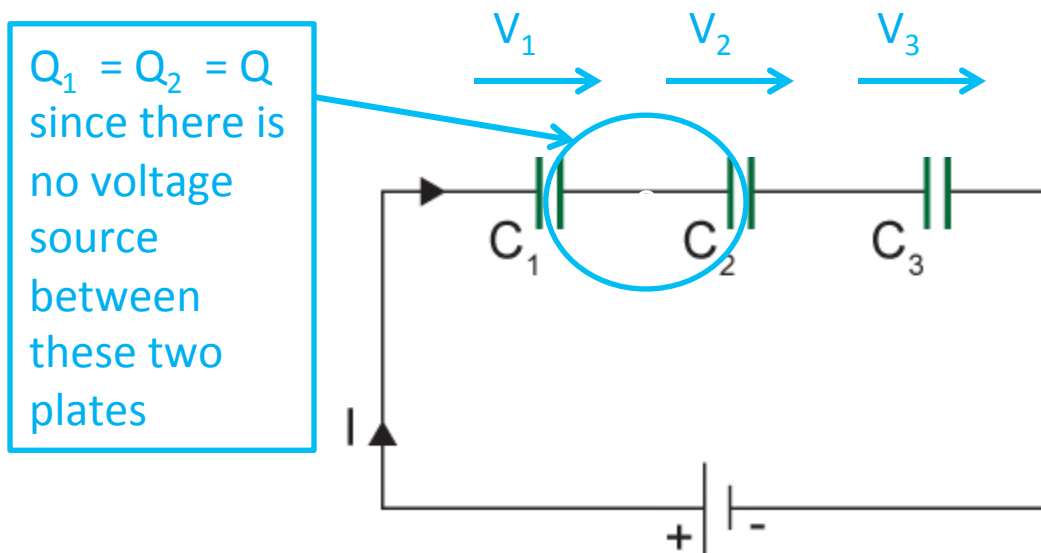


$$V = Q / C_{\text{tot}}$$

$$V_1 = Q / C_1 \quad V_2 = Q / C_2 \quad V_3 = Q / C_3$$


$$V = V_1 + V_2 + V_3 = Q / C_1 + Q / C_2 + Q / C_3$$

$$1 / C_{\text{tot}} = 1 / C_1 + 1 / C_2 + 1 / C_3$$

Measuring resistance

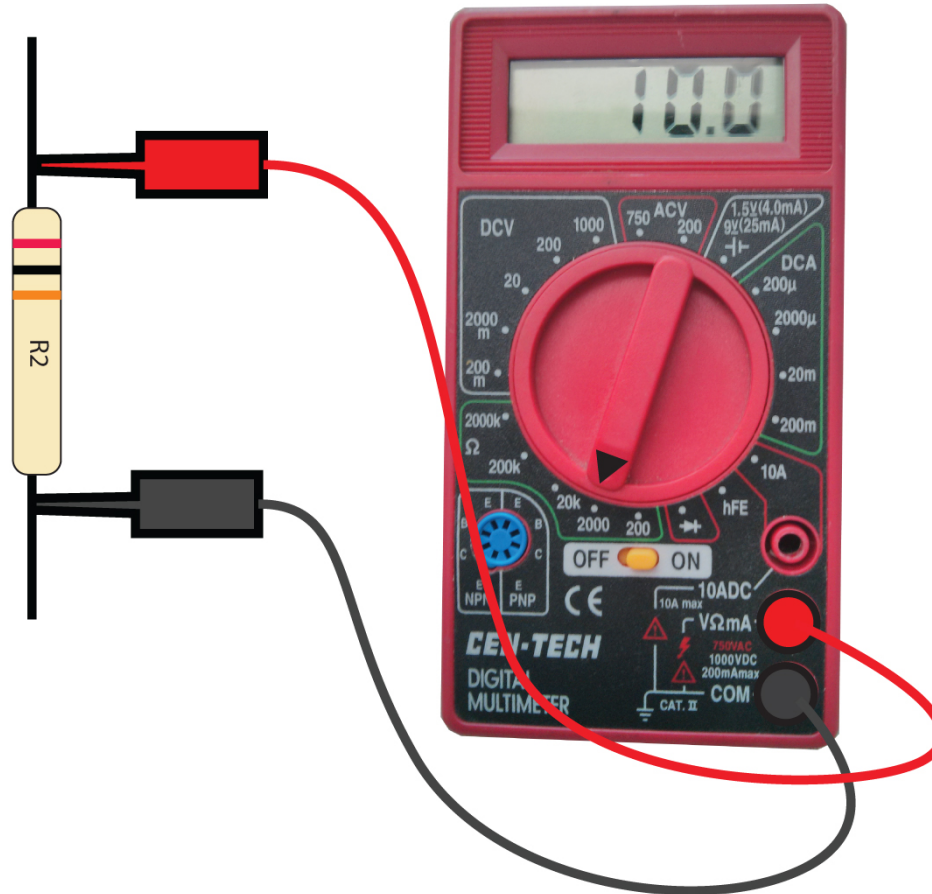


Measuring R with Pasco board

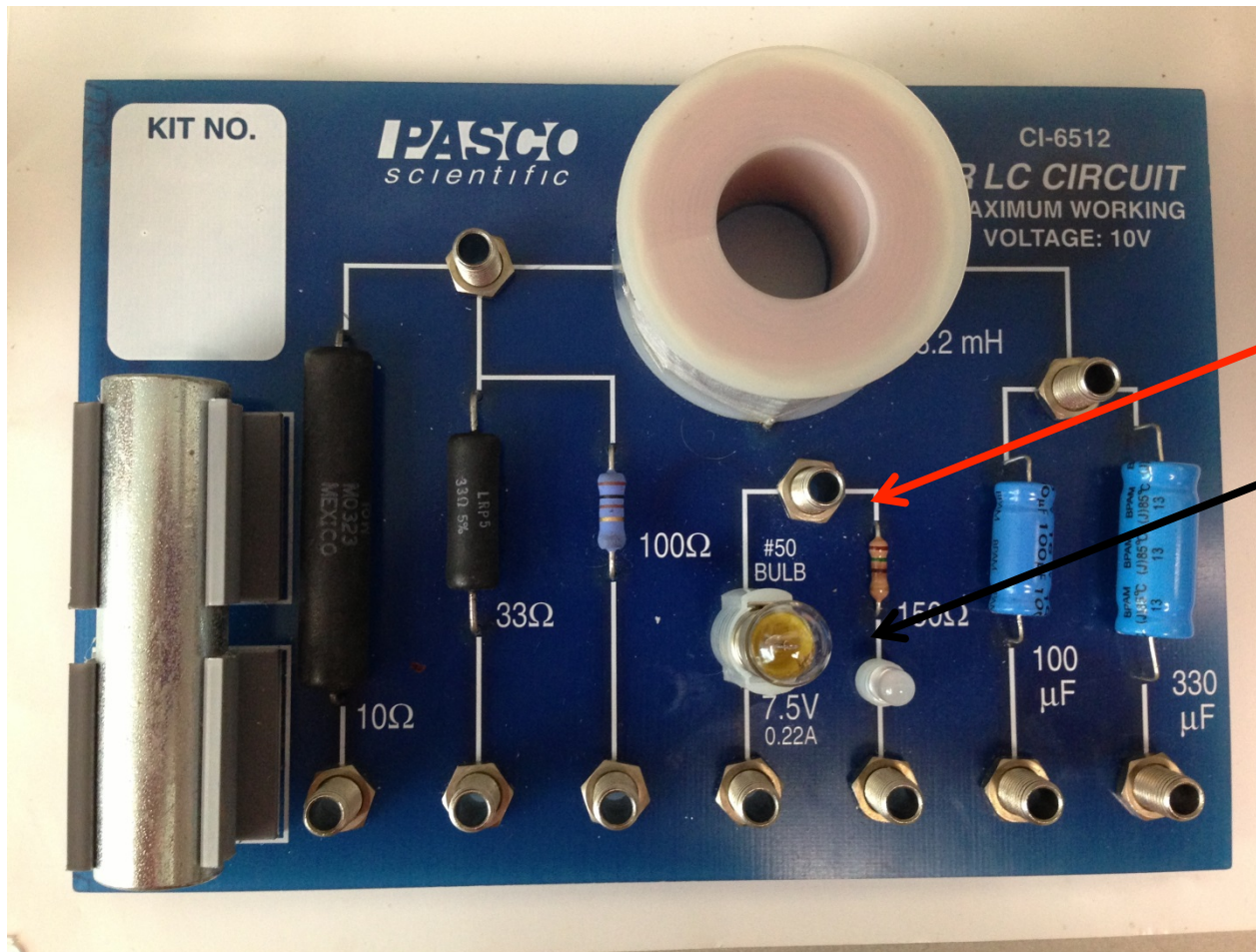

What resistance do you read?


Use patch cords to try some other combinations of the resistors on the left ($10\ \Omega$, $33\ \Omega$ and $100\ \Omega$)

Measuring voltage

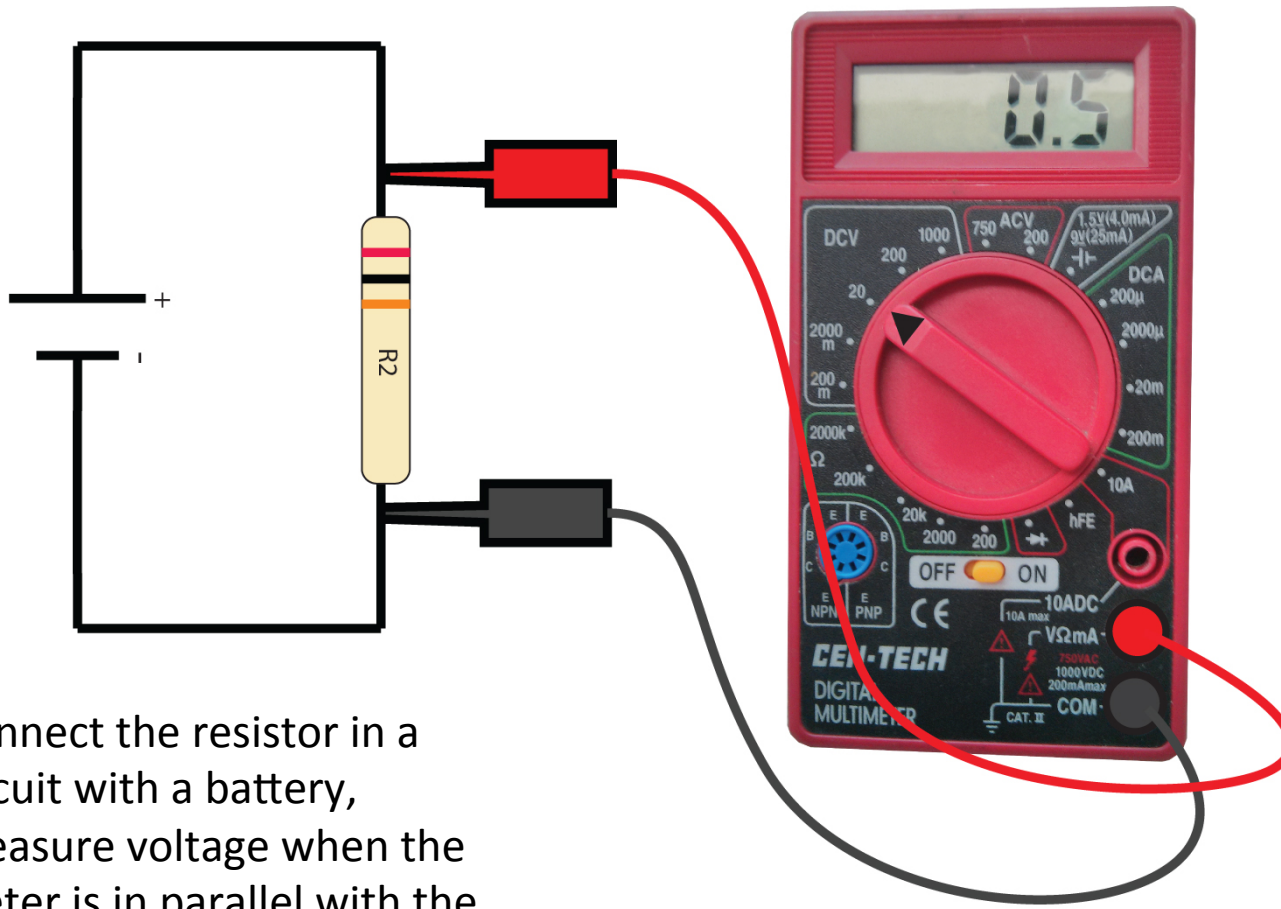

- Connect the resistor in a circuit with a battery,
- Measure voltage when the meter is in parallel with the battery and resistor


Measuring V with Pasco board

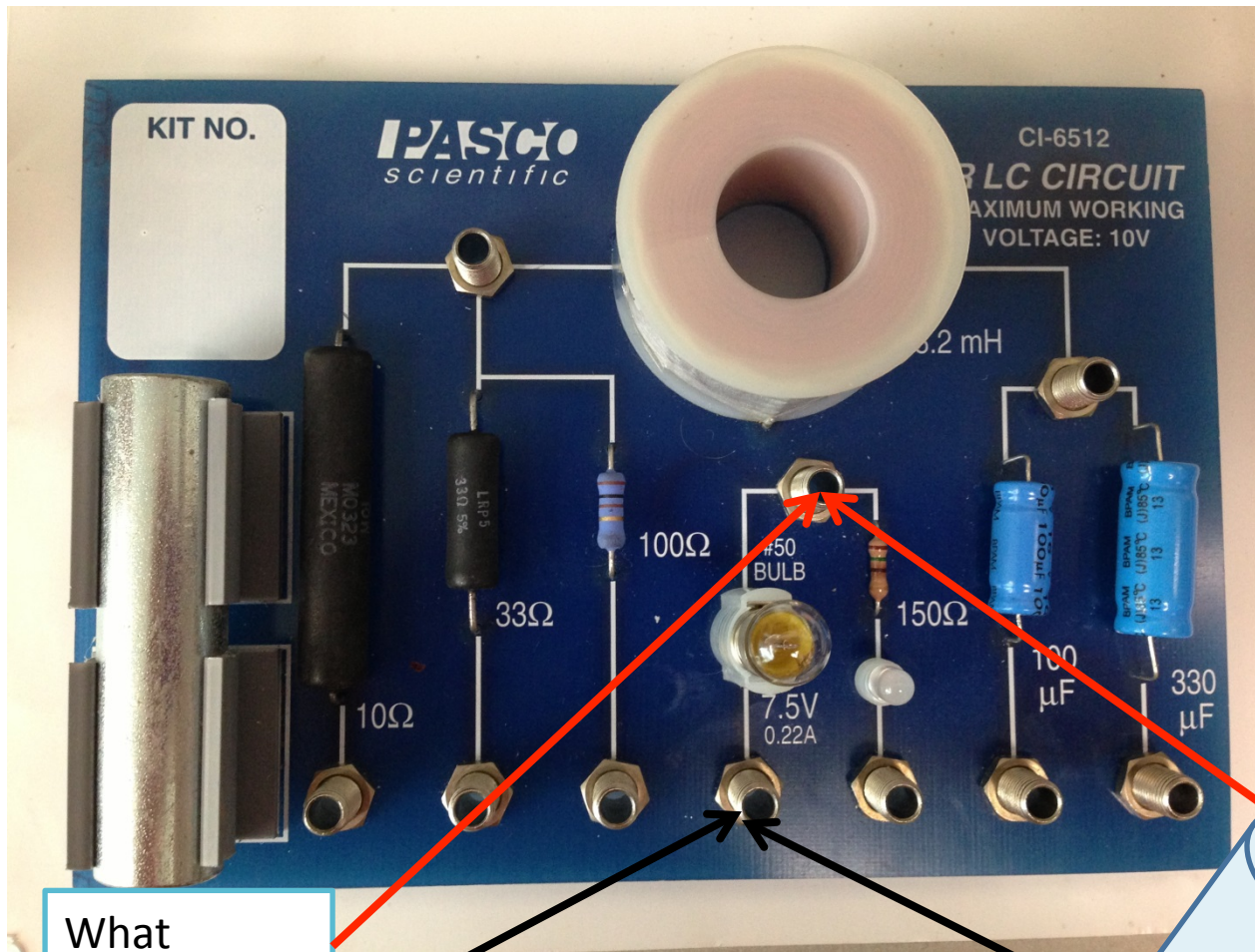

Use patch cords to attach the battery to some of the other combinations of the resistors on the left ($10\ \Omega$, $33\ \Omega$ and $100\ \Omega$)


What voltage do you read?

Measuring current

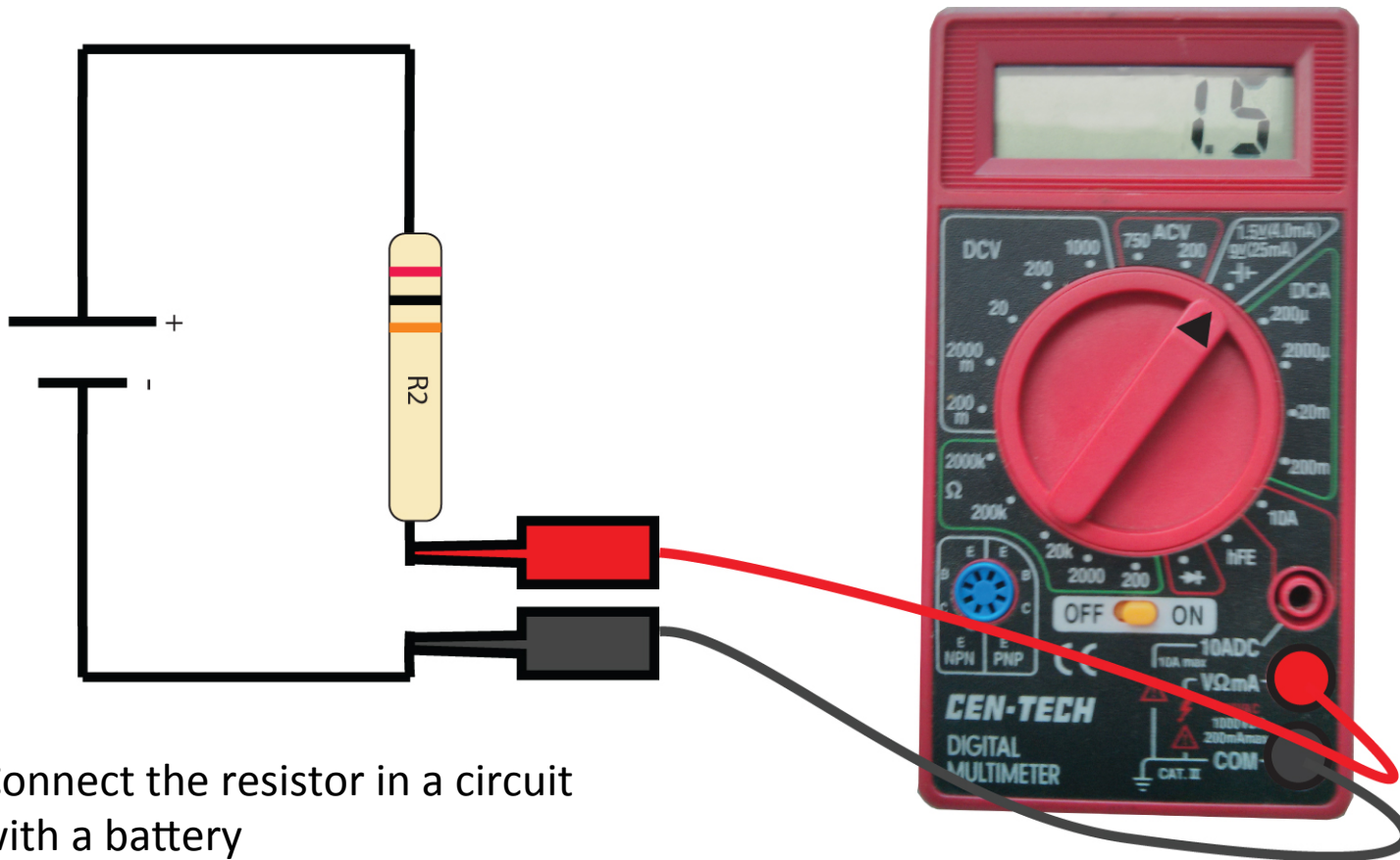

- Connect the resistor in a circuit with a battery
- Measure current when the meter is in series with the battery and resistor


Measuring I with Pasco board

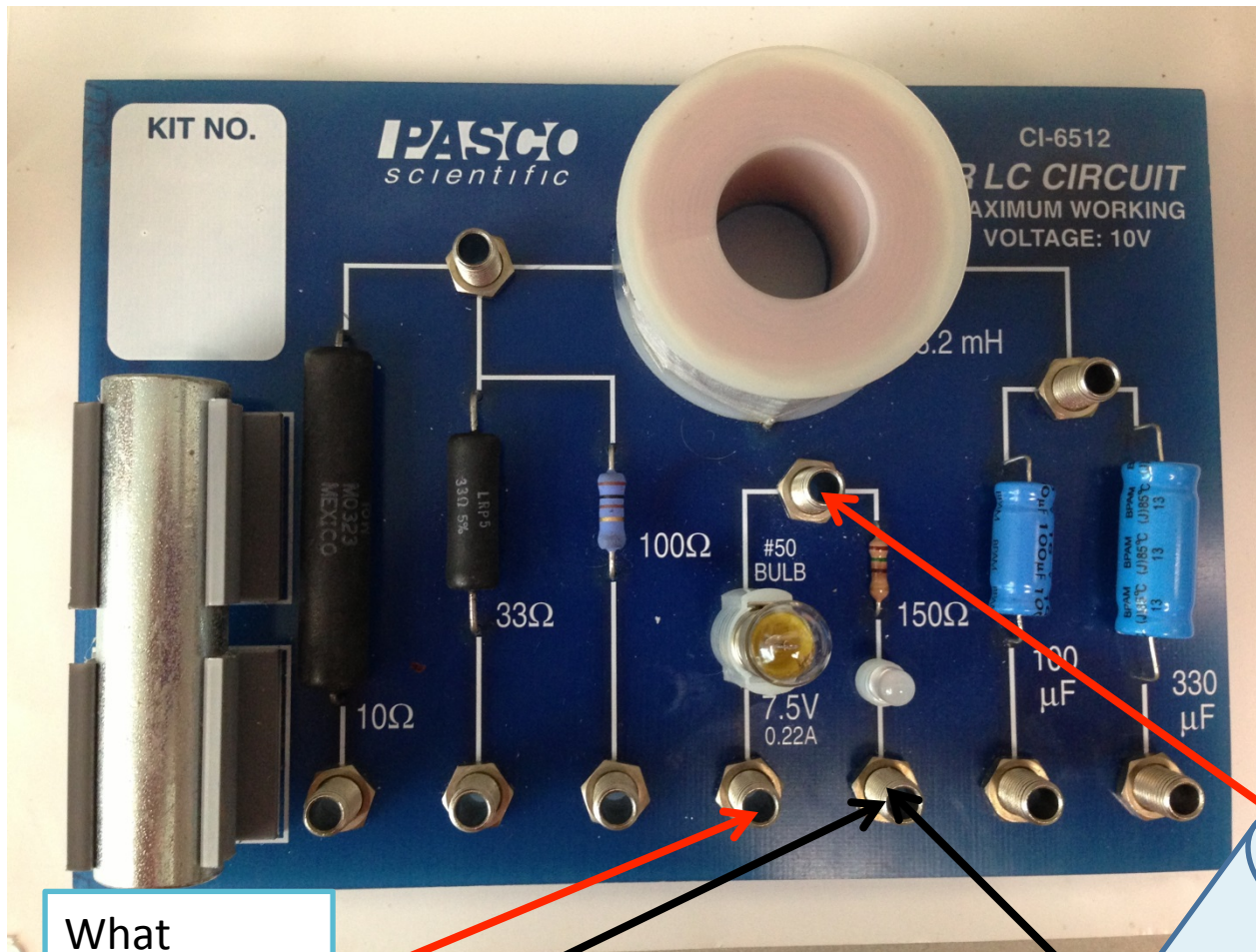

What
current do
you read?

Can you draw
this circuit?

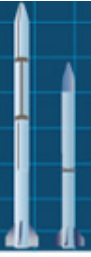If you have time,
try measuring
current with
some of the
other resistors
on the left.



Any questions?

